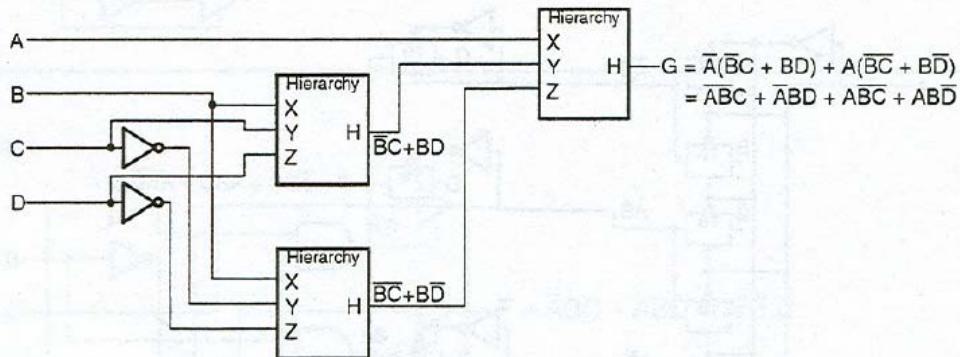


ELEC 204
HW#4 Solutions

3-2.




3-6.

Input	a)	b)
C	1.6ns	1.6ns
D	1.6ns	1.6ns
\overline{B}	1.2ns	1.2ns
A	0.8ns	0.8ns
B	0.8ns	0.8ns
\overline{C}	0.8ns	0.8ns

c) The values are identical in all cases.

3-10.

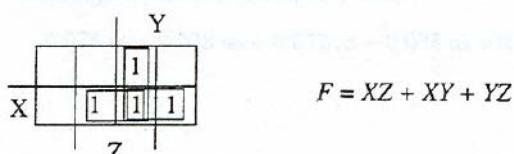

This is the same function as the carry for the full adder.

3-15.

A	B	C	S5	S4	S3	S2	S1	S0	
0	0	0	0	0	0	0	0	0	$S_0 = C$
0	0	1	0	0	0	0	0	1	$S_1 = 0$
0	1	0	0	0	0	1	0	0	$S_2 = \overline{ABC} + ABC$
0	1	1	0	0	1	0	0	1	$S_3 = \overline{ABC} + A\overline{B}C$
1	0	0	0	1	0	0	0	0	$S_4 = A\overline{B} + AC$
1	0	1	0	1	1	0	0	1	$S_5 = AB$
1	1	0	1	0	0	1	0	0	
1	1	1	1	1	0	0	0	1	