

**BİLKENT UNIVERSITY  
ELECTRICAL & ELECTRONICS ENGINEERING  
DEPARTMENT**

**EE 311 ELECTRONICS II**

**Experiment 1**


**Lab Report**

**Biasing and Small Signal Concepts**

**Student Name:**

**ID Number:**

**Date:**

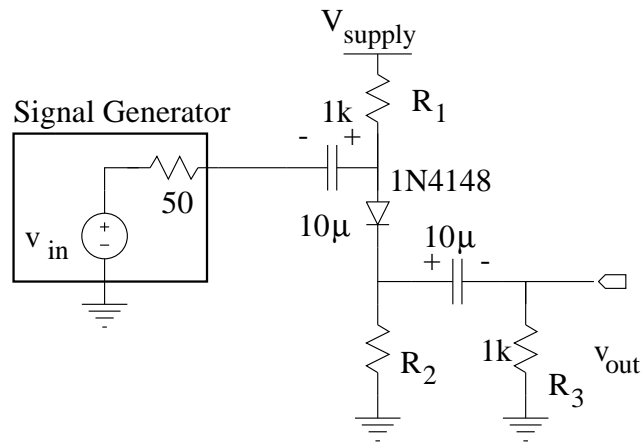

## PRELIMINARY WORK

$v_{in}$  is a sinewave at 2kHz. At this frequency and with this circuit setting, the 10- $\mu$ F decoupling capacitors may be considered as short circuit in AC small signal model.

(a1) Find the AC small-signal model for this frequency for  $V_{supply} = +5V$ , and  $R_2 = 3.9k\Omega$ , and compute the output signal amplitude for  $v_{in}(t) = 100m \sin(2\pi 2K t)V$

(a2) Find the AC small-signal model for this frequency for  $V_{supply} = +5V$ , and  $R_2 = 39k\Omega$ , and compute the output signal amplitude for  $v_{in}(t) = 100m \sin(2\pi 2K t)V$

(a3) Find the AC small-signal model for this frequency for  $V_{supply} = +5V$ , and  $R_2 = 390k\Omega$ , and compute the output signal amplitude for  $v_{in}(t) = 100m \sin(2\pi 2K t)V$

(b) Perform the following SPICE simulations to measure  $v_{out}$ , and append the print-outs to the the end of this report

(b.1) for  $V_{supply} = +5V$  , and  $R_2 = 3.9k\Omega$ ,

(b.1.1) for  $v_{in}(t) = 100m \sin(2\pi 2K t)V$

(b.1.2) for  $v_{in}(t) = 200m \sin(2\pi 2K t)V$

(b.1.3) for  $v_{in}(t) = 500m \sin(2\pi 2K t)V$

(b.1.4) for  $v_{in}(t) = 1 \sin(2\pi 2K t)V$

(b.2) for  $V_{supply} = +5V$  , and  $v_{in}(t) = 100m \sin(2\pi 2K t)V$

(b.2.1) for  $R_2 = 3.9k\Omega$ ,

(b.2.2) for  $R_2 = 39k\Omega$ ,

(b.2.3) for  $R_2 = 390k\Omega$ ,

(b.3) for  $R_2 = 3.9k\Omega$ , and  $v_{in}(t) = 100m \sin(2\pi 2K t)V$

(b.3.1) for  $V_{supply} = +5V$

(b.3.2) for  $V_{supply} = +3V$

(b.3.3) for  $V_{supply} = +2V$

(b.3.4) for  $V_{supply} = +1V$

(c) Explain the circuit operations and List the roles of the components.

**Circuit function:**

**$10 - \mu F$  capacitors:**

**$V_{supply}$ :**

**$R_1$ :**

**$R_2$ :**

**$R_3$ :**

**$D$ :**

(d) **Design**

(d1) Calculations for redesigning the circuit to have the diode small-signal resistance equal  $1k\Omega$ . ( For **Part 4** of the experiment )

(d2) Plan a scheme to verify the design completed in **Part (d1)**.

## EXPERIMENT:

Start with the setting

$$R_2 = 3.9k\Omega$$

$$v_{in}(t) = 100\text{m} \sin(2\pi 2\text{k} t)$$

$$V_{supply} = +5V$$

for parts 1, 2, and 3 in the following.

**Part 1:** Ramp up the amplitude of  $v_{in}$  to 1V. Observe the output waveform and comment on it on the report. Find the maximum allowable amplitude of  $v_{in}$  to have linear operation.

**Observations and comments:**

**Part 2:** Observe the output waveform for

$$R_2 = 3.9k\Omega, \quad 39k\Omega, \quad 390k\Omega$$

cases. Comment on it on the report. Find, by experiment for each case the maximum allowable amplitude of  $v_{in}$  to have linear operation.

**Observations and comments:**

**Part 3:** Ramp down  $V_{supply}$  to 1V in 4 steps. Observe the output waveform and comment on it on the report. Find, by experiment for each case, the maximum allowable amplitude of  $v_{in}$  to have linear operation.

**Observations and comments:**

**Part 4:** Redesign the experimental circuit (find  $R_2$ , or  $V_{supply}$  or both, if necessary) to have the dynamic resistance of the diode equal to  $1k\Omega$ . Verify it by experiment.

**Observations and comments:**