

**BİLKENT UNIVERSITY  
DEPARTMENT OF ELECTRICAL & ELECTRONICS  
ENGINEERING**

**EE 311 ELECTRONICS II**

**Experiment 4**

**Lab Report**

**JFET Source-follower amplifier**

**Student Name:**


**ID Number:**

**Date:**
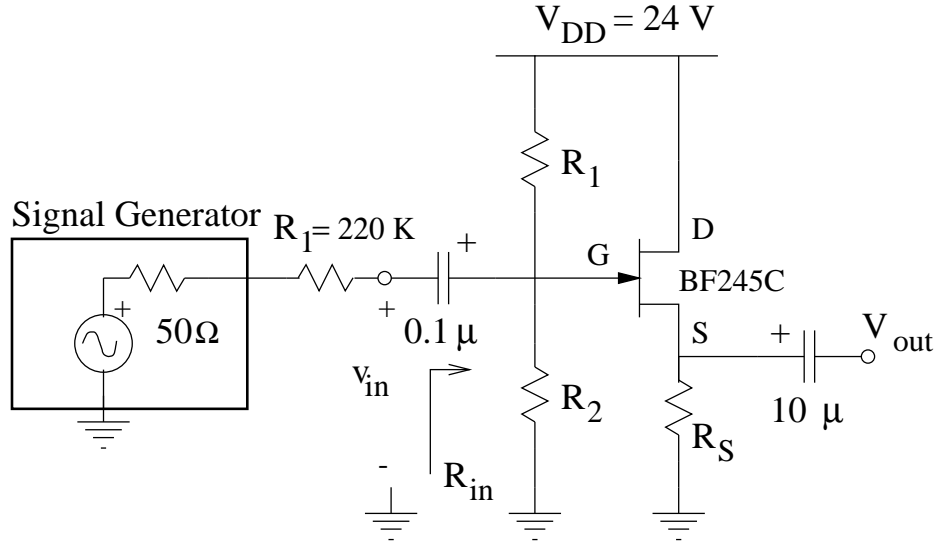
## INTRODUCTION

In this experiment, you will design, construct, and evaluate a single-stage JFET source-follower amplifier that employs self-biasing. Such an amplifier may be used as the output stage of a multistage amplifier to achieve a low output resistance.

You will also generate the  $i_D$  vs  $v_{DS}$  curve of a JFET for various values of  $v_{GS}$ , and measure the transistor parameters  $I_{DSS}$  and  $V_p$ .



## PRELIMINARY WORK

1. Design a single-stage bias-stable JFET amplifier based on the circuit topology given in the figure. In your calculations, assume that the output is not loaded ( $R_L = \infty$ ). The nominal transistor parameters for BF245C are  $V_p = -6.5$  V and  $I_{DSS} = 17$  mA. The following specifications must be met by the circuit:

- Voltage gain  $A_v = v_{out}/v_{in} \geq 0.8$
- Input resistance  $R_{in} \geq 200$  kΩ
- Output resistance  $R_{out} \leq 300$  Ω
- $V_{GSQ} = -3 \pm 1$  V and  $V_{DSQ} = 8 \pm 1$  V

Determine the values of  $R_1$ ,  $R_2$ , and  $R_S$ . Note that you should have  $V_{SQ} > V_{GQ}$  so that the n-channel JFET can be properly biased. Use nominal 10% resistor values only. Try to leave some margin of safety in meeting the above specifications.

The resistor  $R_1$  is included in the circuit to help measure the input resistance  $R_{in}$ . Measuring the AC voltage over  $R_1$  will allow you to determine the AC current  $i_{in}$  at the input of the amplifier. Dividing  $v_{in}$  by  $i_{in}$  will allow you to determine  $R_{in}$ .



2. Generate plots of  $i_D$  vs  $v_{DS}$  and  $i_D$  vs  $v_{GS}$  for the transistor parameters used in part 1. Draw the load line and indicate the  $Q$ -points on these plots. Attach these plots to this report.

3. Analyze the circuit you designed in part 1 for the following transistor parameters and tabulate the results. This will show you how variations in the transistor parameters affect your circuit.

| $V_p$  | $I_{DSS}$ | $V_{GSQ}$ | $I_{DQ}$ | $V_{DSQ}$ | $g_m$ | $R_{out}$ | $A_v$ |
|--------|-----------|-----------|----------|-----------|-------|-----------|-------|
| -6.5 V | 17 mA     |           |          |           |       |           |       |
| -5.0 V | 17 mA     |           |          |           |       |           |       |
| -6.5 V | 15 mA     |           |          |           |       |           |       |
| -5.0 V | 15 mA     |           |          |           |       |           |       |


4. Perform the following SPICE simulations. Append the pages containing the input decks and the results of SPICE simulations to the end of this report.

- (a) Calculate the voltage gain at 2 kHz.
- (b) Calculate the frequency dependence of the voltage gain from 2 Hz to 1 MHz. Determine the lower 3-dB corner frequency.
- (c) Calculate the input resistance at 2 kHz.
- (d) Calculate the output resistance at 2 kHz.

A SPICE model that can be used for transistor BF245C can be found at:  
<http://www.ee.bilkent.edu.tr/~aytur/courses/ee311/labs/bf245c.txt>

## EXPERIMENT:

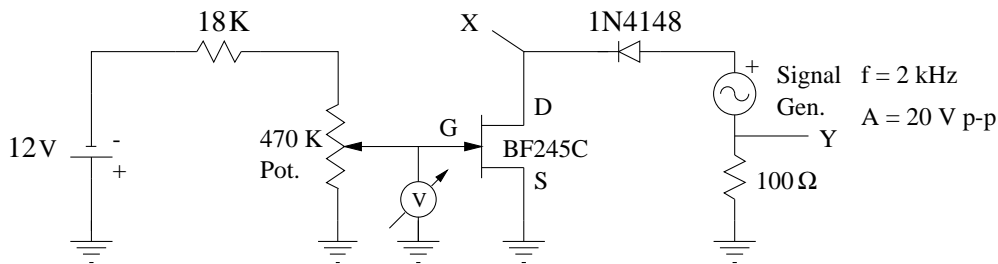1. Construct the following experimental setup to measure the  $i_D$  vs  $v_{DS}$  curve of transistor BF245C for various values of constant  $v_{GS}$ . The 470 k $\Omega$  potentiometer together with the -12 V dc supply are used to set  $v_{GS}$  to any desired value. The signal generator in series with the diode sweeps  $v_{DS}$  approximately in the 0–10 V range. The drain current is measured by reading the voltage across a 100  $\Omega$  resistor. The oscilloscope is used in X-Y mode so that the  $i_D$  vs  $v_{DS}$  curve can be directly seen on the screen.



Generate and plot the  $i_D$  vs  $v_{DS}$  curve for  $V_{GS} = 0, -1, -2, -3, -4, -5, -6, -7$  V. Measure  $I_{DSS}$  by noting the saturation current when  $V_{GS} = 0$  V. To measure  $V_p$ , set  $V_{GS}$  close to where  $I_D \simeq 0$  and change the 100  $\Omega$  resistor with a 10 K $\Omega$  resistor. Then slowly adjust  $V_{GS}$  to determine when  $I_D$  becomes exactly zero to find  $V_p$ .

2. Construct the amplifier that you designed in part 1 of the preliminary work section, and verify that your design meets the specs.

To measure the output resistance  $R_{out}$ , connect a 470  $\Omega$  potentiometer as a load resistor to the amplifier output. Adjust the resistance of the potentiometer while you watch the gain. When the loaded gain is equal to half of the unloaded gain, there is an equal division of output voltage across  $R_{out}$  and  $R_L$ , in which case  $R_{out} = R_L$ . Remove the potentiometer and measure its resistance to find  $R_{out}$ .

Tabulate the measured values of  $V_{GSQ}$ ,  $I_{DQ}$ ,  $V_{DSQ}$ ,  $R_{in}$ ,  $R_{out}$ ,  $A_v$ , and peak-to-peak undistorted output swing.

Call the TA and demonstrate the performance of your circuit. Your circuit must meet the specs before you leave the lab room.