

$$\textcircled{1} \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix} \Rightarrow V_1 = AV_2 + BI_2 \\ I_1 = CV_2 + DI_2$$

Fig. A $A = \frac{V_1}{V_2} \Big|_{I_2=0} \Rightarrow V_2 = \frac{V_1}{z_1 + z_3} \Rightarrow \frac{V_1}{V_2} = \frac{z_1 + z_3}{z_3} \Rightarrow \boxed{A = 1 + z_1/z_3}$

$$B = \frac{V_1}{I_2} \Big|_{V_2=0} \Rightarrow I_2 = \frac{V_1}{z_1 + z_2/z_3} \cdot \frac{1}{z_2} \Rightarrow I_2 = \frac{V_1}{z_1 + \frac{z_2 z_3}{z_2 + z_3}} \cdot \frac{1}{z_2} = \frac{V_1 z_3}{(z_1 z_2 + z_1 z_3 + z_2 z_3)}$$

$$\Rightarrow \frac{V_1}{I_2} = \frac{z_1 z_2 + z_1 z_3 + z_2 z_3}{z_3} \Rightarrow \boxed{B = z_1 + z_2 + \frac{z_1 z_2}{z_3}}$$

$$\boxed{C = \frac{I_1}{V_2} \Big|_{I_2=0} = \frac{1}{z_3}}$$

$$D = \frac{I_1}{I_2} \Big|_{V_2=0} \Rightarrow I_1 \Big|_{V_2=0} = \frac{V_1}{z_1 + \frac{z_2 z_3}{z_2 + z_3}}, \quad I_2 \Big|_{V_2=0} = \frac{V_1}{z_1 + \frac{z_2 z_3}{z_2 + z_3}} \cdot \frac{1}{z_2}$$

$$\Rightarrow \frac{I_1}{I_2} \Big|_{V_2=0} = \frac{\cancel{V_1}}{z_1 + \frac{z_2 z_3}{z_2 + z_3}} \cdot \frac{z_1 + \frac{z_2 z_3}{z_2 + z_3}}{\cancel{V_1}} \cdot \frac{z_2 + z_3}{z_2 z_3} \cdot z_2 = \frac{z_2 + z_3}{z_3}$$

$$\Rightarrow \boxed{D = 1 + z_2/z_3}$$

Fig. B $A = \frac{V_1}{V_2} \Big|_{I_2=0}$ let I_x be the current passing through Y_3 & $Y_2 \Rightarrow V_1 = I_x \left(\frac{1}{Y_3} + \frac{1}{Y_2} \right)$
 $V_2 = I_x / Y_2$

$$\Rightarrow \frac{V_1}{V_2} \Big|_{I_2=0} = \frac{1/Y_2 + 1/Y_3}{1/Y_2} = \frac{Y_2 + Y_3}{Y_3} \Rightarrow \boxed{A = 1 + \frac{Y_2}{Y_3}}$$

$$B = \frac{V_1}{I_2} \Big|_{V_2=0} \Rightarrow V_1 = \frac{I_2}{Y_3} \Rightarrow \boxed{B = \frac{1}{Y_3}}$$

$$C = \frac{I_1}{V_2} \Big|_{I_2=0} \Rightarrow \frac{I_1}{V_1} = Y_1 + \frac{Y_2 Y_3}{Y_2 + Y_3} \quad (*) \quad \text{also } V_2 = V_1 \left(\frac{Y_3}{Y_2 + Y_3} \right) \Rightarrow V_1 = \frac{V_2 (Y_2 + Y_3)}{Y_3} \quad (**)$$

$$\text{from } (*) \text{ \& } (**) \quad I_1 = \left(Y_1 + \frac{Y_2 Y_3}{Y_2 + Y_3} \right) \left(\frac{Y_2 + Y_3}{Y_3} \right) V_2 \Rightarrow \frac{I_1}{V_2} \Big|_{I_2=0} = \frac{Y_1 Y_2 + Y_1 Y_3 + Y_2 Y_3}{Y_3}$$

$$\Rightarrow \boxed{C = Y_1 + Y_2 + \frac{Y_1 Y_2}{Y_3}}$$

$$D = \frac{I_1}{I_2} \Big|_{V_2=0} = \frac{I_1 - I_2}{Y_1} = \frac{I_2}{Y_3} \Rightarrow I_1 = I_2 + I_2 \frac{Y_1}{Y_3} \Rightarrow \boxed{D = 1 + \frac{Y_1}{Y_3}}$$

Note that for both figures, you can find $\begin{bmatrix} A & B \\ C & D \end{bmatrix}$ as the cascade connection of 3 2-port networks! Can you verify it?

② $\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix} \Rightarrow A = \frac{V_1}{V_2} \Big|_{I_2=0} \Rightarrow \text{port 2 is o.c.}$

$$\left. \begin{aligned} V_1 \Big|_{I_2=0} &= v^+ e^{j\beta l} + v^- e^{-j\beta l} \\ V_2 \Big|_{I_2=0} &= v^+ + v^- \end{aligned} \right\} \frac{V_1}{V_2} = \frac{v^+ e^{j\beta l} + v^- e^{-j\beta l}}{v^+ + v^-} \quad \text{but port 2 is o.c.} \\ \Rightarrow \Gamma = 1 \Rightarrow v^+ = v^-$$

$$\Rightarrow A = \frac{V_1}{V_2} \Big|_{I_2=0} = \frac{v^+ (e^{j\beta l} + e^{-j\beta l})}{2v^+} = \cos \beta l \Rightarrow \boxed{A = \cos \beta l}$$


$$B = \frac{V_1}{I_2} \Big|_{V_2=0} \Rightarrow \text{port 2 is s.c.} = \frac{v^+ e^{j\beta l} + v^- e^{-j\beta l}}{\frac{v^+}{Z_0} - \frac{v^-}{Z_0}} \quad \text{but } v^+ = -v^- \Rightarrow B = \frac{v^+ (e^{j\beta l} - e^{-j\beta l})}{2v^+ / Z_0}$$

$$\Rightarrow \boxed{B = j Z_0 \sin \beta l}$$

$$C = \frac{I_1}{V_2} \Big|_{I_2=0} = \frac{v^+ / Z_0 (e^{j\beta l} - e^{-j\beta l})}{2v^+} = \boxed{j Y_0 \sin \beta l = C}$$

$$D = \frac{I_1}{I_2} \Big|_{V_2=0} = \frac{v^+ / Z_0 e^{j\beta l} - v^- / Z_0 e^{-j\beta l}}{\frac{v^+}{Z_0} - \frac{v^-}{Z_0}} \quad \text{but } v^+ = -v^- \Rightarrow D = \frac{I_1}{I_2} \Big|_{V_2=0} = \frac{\frac{v^+}{Z_0} (e^{j\beta l} + e^{-j\beta l})}{\frac{v^+}{Z_0} 2}$$

$$\Rightarrow \boxed{D = \cos \beta l}$$

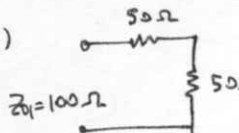
③ (a)  $S_{11} = \Gamma_{in} = \frac{100 - Z_{01}}{100 + Z_{01}} \quad \text{but } Z_{01} = 100 \Omega \Rightarrow \boxed{S_{11} = 0}$


(b)  $S_{22} = \Gamma_{out} = \frac{150 - Z_{02}}{150 + Z_{02}} = \frac{100}{200} \Rightarrow \boxed{S_{22} = 1/2}$

(c) $S_{21} = \frac{b_2}{a_1} \Big|_{a_2=0} \quad I_1 = -I_2 = \frac{1}{\sqrt{Z_{01}}} (a_1 - b_1) = -\frac{1}{\sqrt{Z_{02}}} (a_2 - b_2) \quad \begin{aligned} a_2 &= 0 \text{ (for } S_{21}) \\ b_1 &= 0 \text{ since } S_{11} = 0 \end{aligned}$

$$\Rightarrow S_{21} = \frac{b_2}{a_1} = \sqrt{\frac{Z_{02}}{Z_{01}}} = \sqrt{\frac{50}{100}} = \frac{1}{\sqrt{2}}$$

(d) $S_{12} = S_{21}$ due to reciprocity (we have a simple resistor)

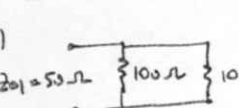④ (a)  $\Rightarrow \boxed{S_{11} = 0}$

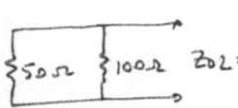(b)  $Z_{02} = 100 \Omega$

$$S_{22} = \frac{100/3 - 100}{100/3 + 100} \Rightarrow \boxed{S_{22} = -1/2}$$

(c) $S_{21} = \frac{b_2}{a_1} \Big|_{a_2=0} \quad V_1 = V_2 \Rightarrow \sqrt{50} (a_1 - b_1) = \sqrt{100} (a_2 + b_2) \quad \Rightarrow S_{21} = \frac{b_2}{a_1} \Big|_{a_2=0} = \sqrt{\frac{50}{100}} = \frac{1}{\sqrt{2}}$

since $S_{11} = 0$

(d) $S_{12} = S_{21}$ since device is reciprocal

⑤ $S = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix}$ $[S]$ is reciprocal $\Rightarrow S_{12} = S_{21}$, $[S]$ is unitary $\Rightarrow$ network is lossless

$$\left. \begin{aligned} |S_{11}|^2 + |S_{12}|^2 &= 1 & \text{--- (a)} \\ S_{11} S_{12}^* + S_{12} S_{22}^* &= 0 & \text{--- (b)} \\ |S_{12}|^2 + |S_{22}|^2 &= 1 & \text{--- (c)} \end{aligned} \right\} \text{from (a) \& (c) } |S_{11}|^2 = |S_{22}|^2 \Rightarrow |S_{11}| = |S_{22}|$$

then $|S_{12}| = \sqrt{1 - |S_{11}|^2}$

$$\left. \begin{aligned} S_{11} &= |S_{11}| e^{j\theta_1} \\ S_{22} &= |S_{22}| e^{j\theta_2} = |S_{11}| e^{j\theta_1} \\ S_{12} &= S_{21} = |S_{12}| e^{j\phi_1} = (1 - |S_{11}|^2)^{1/2} e^{j\phi_1} \end{aligned} \right\} \text{use these eqns. together with eqn. (b)}$$

$$\Rightarrow |S_{11}| e^{j\theta_1} (1 - |S_{11}|^2)^{1/2} e^{-j\phi_1} + (1 - |S_{11}|^2)^{1/2} e^{j\phi_1} |S_{11}| e^{-j\theta_2} = 0$$

$$\Rightarrow |S_{11}| [1 - |S_{11}|^2]^{1/2} \underbrace{\left[e^{j\theta_1} e^{-j\phi_1} + e^{j\phi_1} e^{-j\theta_2} \right]}_{=0} = 0 \Rightarrow e^{j\theta_1} e^{-j\phi_1} = -e^{j\phi_1} e^{-j\theta_2} \Rightarrow e^{j(\theta_2 + \theta_1)} = -e^{j2\phi_1}$$

$$\Rightarrow \phi_1 = \frac{\theta_1 + \theta_2}{2} + \frac{\pi}{2} + n\pi$$

⑥ (a) If all ports are matched, there is no reflection $\Rightarrow S_{ii} = 0$ for $i = 1, 2, 3$

(b) If network is reciprocal, then $S_{ij} = S_{ji} \Rightarrow [S] = \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{12} & 0 & S_{23} \\ S_{13} & S_{23} & 0 \end{bmatrix}$ and if the network is lossless, then $[S]$ matrix is unitary.

$$\left. \begin{aligned} |S_{12}|^2 + |S_{13}|^2 &= 1 & \text{--- (1)} \\ |S_{12}|^2 + |S_{23}|^2 &= 1 & \text{--- (2)} \\ |S_{13}|^2 + |S_{23}|^2 &= 1 & \text{--- (3)} \end{aligned} \right\} \Rightarrow \text{From (1)-(3) at least two of the three parameters } (S_{12}, S_{13}, S_{23}) \text{ must be zero.}$$

$$\left. \begin{aligned} S_{13}^* S_{23} &= 0 & \text{--- (4)} \\ S_{23}^* S_{12} &= 0 & \text{--- (5)} \\ S_{12}^* S_{13} &= 0 & \text{--- (6)} \end{aligned} \right\}$$


However, this condition is inconsistent with equations (a)-(c) implying that a three-port network can not be lossless, reciprocal and matched at all ports.

(c) $[S] = \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{21} & 0 & S_{23} \\ S_{31} & S_{32} & 0 \end{bmatrix}$, network is lossless $\Rightarrow [S]$ is unitary $\Rightarrow$

$$\left. \begin{aligned} |S_{12}|^2 + |S_{32}|^2 &= 1 & S_{31}^* S_{32} &= 0 \\ |S_{21}|^2 + |S_{31}|^2 &= 1 & S_{21}^* S_{23} &= 0 \\ |S_{13}|^2 + |S_{23}|^2 &= 1 & S_{12}^* S_{13} &= 0 \end{aligned} \right\}$$

$$\Rightarrow S_{32} = 1, S_{13} = 1, S_{21} = 1 \Rightarrow [S] = \begin{bmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{bmatrix}$$

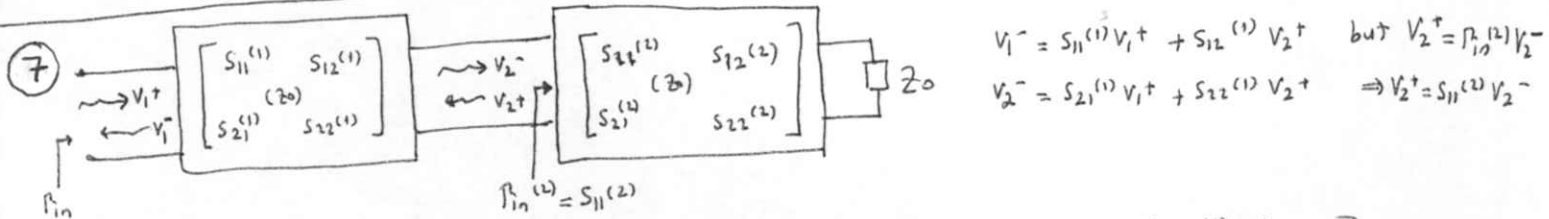$[S]$ matrix of a lossless circulator which works in the clockwise direction.



$$\Rightarrow V_1^- = S_{11}^{(1)} V_1^+ + S_{12}^{(1)} S_{11}^{(2)} V_2^-$$

$$V_2^- = S_{21}^{(1)} V_1^+ + S_{22}^{(1)} S_{11}^{(2)} V_2^- \Rightarrow V_2^- = \frac{S_{21}^{(1)} V_1^+}{1 - S_{22}^{(1)} S_{11}^{(2)}}$$

$$\Rightarrow V_1^- = V_1^+ \left[S_{11}^{(1)} + S_{11}^{(2)} \frac{S_{12}^{(1)} S_{21}^{(1)}}{1 - S_{11}^{(2)} S_{22}^{(1)}} \right] \Rightarrow \Gamma_{in} = \frac{V_1^-}{V_1^+} = S_{11}^{(1)} + S_{11}^{(2)} \frac{S_{12}^{(1)} S_{21}^{(1)}}{1 - S_{11}^{(2)} S_{22}^{(1)}}$$