
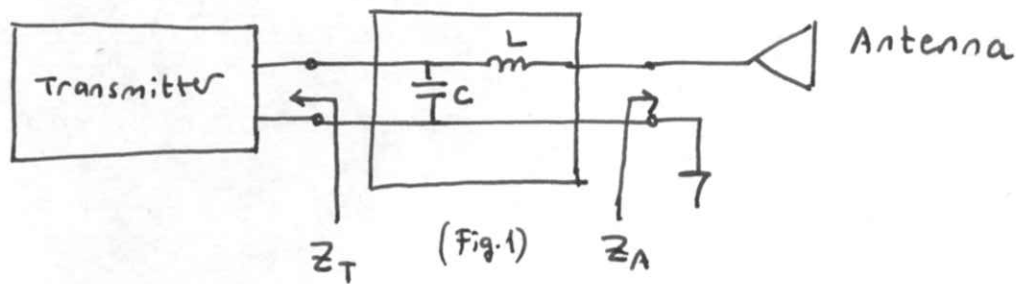


①

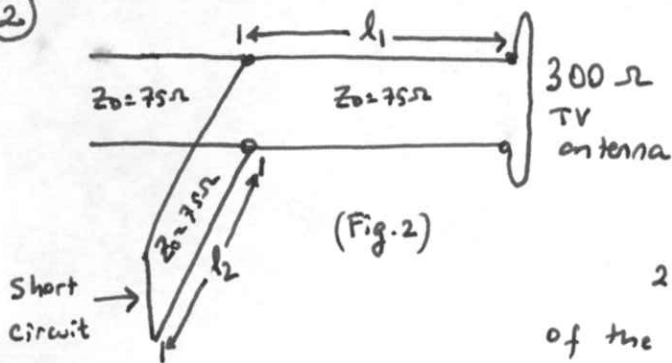


The output impedance of a transmitter operating at a frequency of 2 GHz is $Z_T = 150 + j75 \Omega$. Design an L-section matching network, as shown in the figure, such that the maximum power is delivered to the antenna whose input impedance is $Z_A = 75 + j15 \Omega$. Note that the characteristic impedance Z_0 is not given. Therefore, you can select a random Z_0 since it does not affect your solution. Choose $Z_0 = 75 \Omega$ for simplicity. (Hint: For this problem Z_T should be matched to Z_A^*)

②



The arrangement shown in Fig. 2 is used to match a 300 Ω TV antenna to a receiver having a 75 Ω input. The 75 Ω transmission line has a propagation velocity of 2×10^8 m/sec. Determine the smallest values of the lengths l_1 and l_2 which will achieve matching. The frequency is 90 MHz.

③

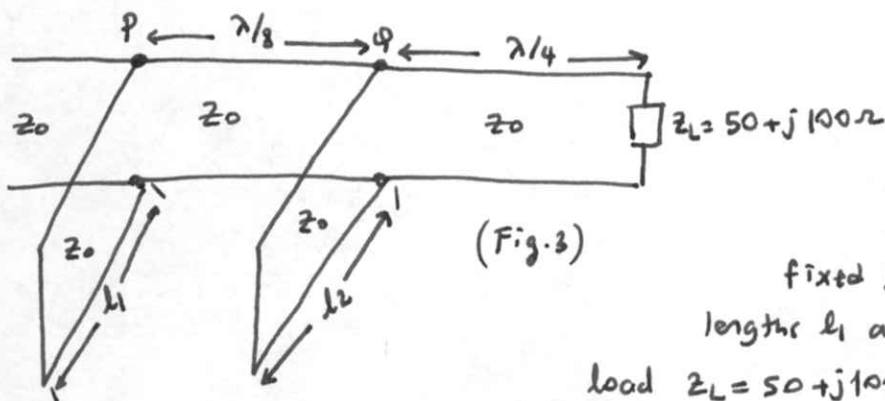

A double-stub tuner is illustrated in Fig. 3, where the positions of the stubs on the transmission line are fixed but the short-circuited stub lengths l_1 and l_2 are variable. If the load $Z_L = 50 + j100 \Omega$ and the characteristic impedances of the line and stubs are both $Z_0 = 100 \Omega$, determine the shortest lengths l_1 and l_2 to give no reflected wave at point P.