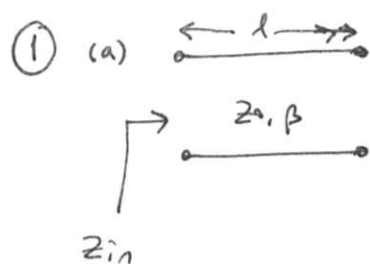


Solutions to HW # 4

①




$$Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)} \quad \text{if } Z_L \rightarrow \infty$$

$$\Rightarrow Z_{in} = -jZ_0 \cot(\beta l) = -j \frac{Z_0}{\tan(\beta l)}$$

if $\beta l \ll 1 \Rightarrow \tan(\beta l) \approx \beta l$

$$\Rightarrow Z_{in} \approx -j \frac{Z_0}{\beta l} \quad \text{use } Z_0 = \sqrt{\frac{L}{C}} \quad \text{and } \beta = \omega \sqrt{LC}$$
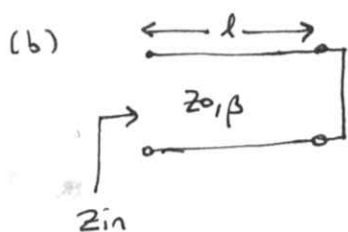
$$\Rightarrow Z_{in} \approx -j \sqrt{\frac{L}{C}} \frac{1}{\omega \sqrt{LC}} \frac{1}{l} \Rightarrow -j \frac{1}{\omega C l} \quad \text{where } Cl \text{ equivalent impedance}$$



$$Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)} \quad \text{if } Z_L \rightarrow 0$$

$$\Rightarrow Z_{in} = jZ_0 \tan(\beta l) \quad \text{if } \beta l \ll 1 \Rightarrow \tan(\beta l) \approx \beta l$$

$$\Rightarrow Z_{in} \approx jZ_0 \beta l = j \sqrt{\frac{L}{C}} \omega \sqrt{LC} l = j\omega L l \quad \text{where } L l: \text{ equivalent inductance}$$

②
$$\left. \begin{aligned} Z_{in}^{oc} &= -jZ_0 \cot(\beta l) \\ Z_{in}^{sc} &= jZ_0 \tan(\beta l) \end{aligned} \right\} \Rightarrow Z_{in}^{oc} Z_{in}^{sc} = Z_0^2 \Rightarrow \boxed{Z_0 = \sqrt{Z_{in}^{oc} Z_{in}^{sc}}}$$

$$\Rightarrow \frac{Z_{in}^{sc}}{Z_{in}^{oc}} = \frac{jZ_0 \tan(\beta l)}{-jZ_0 \cot(\beta l)} = -\tan^2(\beta l) \Rightarrow \tan(\beta l) = \sqrt{-\frac{Z_{in}^{sc}}{Z_{in}^{oc}}}$$

$$\Rightarrow \boxed{\beta = \frac{1}{l} \tan^{-1} \sqrt{-\frac{Z_{in}^{sc}}{Z_{in}^{oc}}}}$$

③

$$V(z) = V^+ e^{-j\beta z} + V^- e^{j\beta z} \Rightarrow V(z) = V^+ (e^{-j\beta z} + \Gamma_L e^{j\beta z}) \quad \text{with } \Gamma_L = \frac{R_L - \sqrt{Z_0 R_L}}{R_L + \sqrt{Z_0 R_L}}$$

$$V(z=-l) = V^+ (e^{j\beta l} + \Gamma_L e^{-j\beta l}) = V_i$$

$$\Rightarrow \boxed{V^+ = \frac{V_i}{(e^{j\beta l} + \Gamma_L e^{-j\beta l})}} \Rightarrow \boxed{V^- = \Gamma_L \frac{V_i}{(e^{j\beta l} + \Gamma_L e^{-j\beta l})}}$$

OR (second method)

$$V(z) = V^+ e^{-j\beta(z+l)} + V^- e^{j\beta(z+l)}$$

$$V(z=-l) = V_i = V^+ + V^- \quad , \quad V(z=0) = V^+ e^{-j\beta l} + V^- e^{j\beta l}$$

$$\Gamma_L = \frac{V^- e^{j\beta l}}{V^+ e^{-j\beta l}} \Rightarrow V^- = \Gamma_L V^+ e^{-j\beta l 2}$$

$$V_i = V^+ + \Gamma_L V^+ e^{-j\beta l 2} = V^+ (1 + \Gamma_L e^{-j\beta l 2}) \Rightarrow \boxed{V^+ = \frac{V_i}{1 + \Gamma_L e^{-j\beta l 2}}}$$

$$\Rightarrow \boxed{V^- = \frac{\Gamma_L e^{-j\beta l 2} V_i}{1 + \Gamma_L e^{-j\beta l 2}}}$$

Note that even if the V^+ & V^- expressions found using a different reference (second method) are different than the first method, notice that $V(z)$ expression is same in both methods

1st way: $V(z) = V^+ e^{-j\beta z} + V^- e^{j\beta z} \Rightarrow \boxed{V(z) = \frac{V_i e^{-j\beta z}}{(e^{j\beta l} + \Gamma_L e^{-j\beta l})} + \Gamma_L \frac{V_i e^{j\beta z}}{(e^{j\beta l} + \Gamma_L e^{-j\beta l})}}$

2nd way: $V(z) = V^+ e^{-j\beta(z+l)} + V^- e^{j\beta(z+l)}$

$$\Rightarrow V(z) = \frac{V_i e^{-j\beta z} e^{-j\beta l}}{(1 + \Gamma_L e^{-j\beta l 2})} + \frac{\Gamma_L e^{-j\beta l 2} V_i e^{j\beta z} e^{j\beta l}}{(1 + \Gamma_L e^{-j\beta l 2})}$$

$$\Rightarrow \boxed{V(z) = \frac{V_i e^{-j\beta z}}{(e^{j\beta l} + \Gamma_L e^{-j\beta l})} + \Gamma_L \frac{V_i e^{j\beta z}}{(e^{j\beta l} + \Gamma_L e^{-j\beta l})}}$$

same

Solutions to HW #4

④ $f = 1 \text{ GHz} \Rightarrow \lambda_0 = \frac{c}{f} = 30 \text{ cm} \Rightarrow \lambda_1 = 7.5 \text{ cm} \Rightarrow \lambda_1 = \frac{\lambda_0}{4} \text{ QWT}$
 $\Rightarrow \lambda_1 = \frac{c/\sqrt{\epsilon_r}}{f} = 15 \text{ cm} \Rightarrow \lambda_2 = 7.5 \text{ cm} \Rightarrow \lambda_2 = \frac{\lambda}{2} \text{ Half wave transformer}$


$\text{SWR} = 2 = \frac{1+|\Gamma|}{1-|\Gamma|} \Rightarrow |\Gamma| = \frac{1}{3} \quad (Z_{Li} > Z_0 \text{ \& } Z_{Li} \text{ are real for } i=1,2)$

$\Rightarrow \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{1}{3} \Rightarrow Z_L = 100 \Omega$

For λ_1 if $Z_{L1} = 100 \Omega \Rightarrow Z_{in1} = \frac{Z_0^2}{Z_L} = \frac{50 \times 50}{100} = 25 \Omega \quad (\text{QWT})$

For λ_2 if $Z_{L2} = 100 \Omega \Rightarrow Z_{in2} = Z_{L2} = 100 \Omega \quad (\text{Half-wave transformer})$

Then, the equivalent ckt. becomes

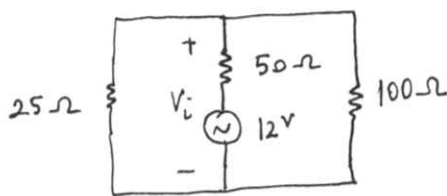

$\Rightarrow V_i = \frac{12 \text{ V}}{50 + 100//25} = \frac{24}{7} \text{ V}$

$P_1 = \frac{1}{2} \frac{|V_i|^2}{R_1} = \frac{1}{2} \left(\frac{24}{7} \right)^2 \frac{1}{25} = \frac{0.47}{2} \text{ Watts} \quad \left(\text{On the quarter wave section} \right)$

$P_2 = \frac{1}{2} \frac{|V_i|^2}{R_2} = \frac{1}{2} \left(\frac{24}{7} \right)^2 \frac{1}{100} = \frac{0.12}{2} \text{ watts} \quad \left(\text{On the half-wave section} \right)$

⑤ $V_i = V_0^+ \left(e^{-j\beta z} + \Gamma_L e^{j\beta z} \right) \Big|_{z=-l} = V_0^+ e^{-j\beta l} \left(1 + \Gamma_L e^{j2\beta l} \right) \Big|_{z=-l}$

where $V_0^+ = V_g \frac{Z_0}{Z_0 + Z_g} \frac{e^{-j\beta l}}{[1 - \Gamma_L \Gamma_g e^{-j2\beta l}]}$

with $\Gamma_g = \frac{Z_g - Z_0}{Z_g + Z_0} = 0, \quad \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = 0.447 + j0.648$

$\beta = \frac{\omega}{c} = \frac{2\pi \times 10^8}{3 \times 10^8} = \frac{2\pi}{3} \text{ rad/m} \Rightarrow \beta l = 2.4\pi$

$\Rightarrow V_i = V_g \frac{Z_0}{Z_0 + Z_g} e^{-j\beta l} e^{j\beta l} \left(1 + \Gamma_L e^{-j2\beta l} \right) = 10 \frac{50}{100} e^{-j2.4\pi} e^{j2.4\pi} \left(1 + 0.447 e^{j0.648\pi} e^{-j4.8\pi} \right)$

$\Rightarrow V_i = 7.06 \angle -8.43^\circ \text{ (V)}$

(b) $V_L = V(0) = V_0^+ (1 + \Gamma_L) = V_g \frac{Z_0}{Z_0 + Z_g} e^{-j\beta l} (1 + \Gamma_L) = 10 \frac{50}{100} e^{-j2.4\pi} \left(1 + 0.447 e^{j0.648\pi} \right)$

$\Rightarrow V_L = 4.47 \angle -45.5^\circ \text{ (V)}$

(d) $P_{ave} = \frac{1}{2} \left| \frac{V_L}{Z_L} \right|^2 R_L = \frac{1}{2} \left(\frac{4.47}{35.36} \right)^2 25 = 0.2 \text{ W}$

(c) $V_{SWR} = \frac{1+|\Gamma_L|}{1-|\Gamma_L|} = \frac{1+0.447}{1-0.447} = 2.62$

(a) $\alpha = 1.5 \text{ dB/m} \Rightarrow \alpha = \frac{1.5}{8.686} \text{ Np/m}$ (This conversion is necessary, since the unit of α is Np/m)

$$\gamma = \alpha + j\beta, \quad \beta = \frac{2\pi}{\lambda} = \frac{2\pi f}{c} = 20.944 \text{ rad/m}$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{1}{3}, \quad \Gamma_g = \frac{Z_g - Z_0}{Z_g + Z_0} = 0$$

$$\Rightarrow V_o^+ = V_g \frac{Z_0}{Z_0 + Z_g} \frac{e^{-\gamma l}}{[1 - \Gamma_L \Gamma_g e^{-2\gamma l}]} \Rightarrow V_o^+ = V_g \frac{Z_0}{Z_0 + Z_g} e^{-\gamma l}$$

$$\Rightarrow P_{in} = \frac{|V_o^+|^2}{2Z_0} [e^{2\alpha l} - |\Gamma_L|^2 e^{-2\alpha l}] = 0.243/2 \text{ Watts}$$

$$\Rightarrow P_L = \frac{|V_o^+|^2}{2Z_0} [1 - |\Gamma_L|^2] = \frac{0.111}{2} \text{ Watts}$$

(b) Return loss = $10 \log \frac{1}{|\Gamma|^2} \Rightarrow$ At the input $|\Gamma_{in}| = |\Gamma_L| e^{-2\alpha l}$

$$RL_{input} = 10 \log_{10} \frac{1}{|\Gamma_{in}|^2} = 15.542 \text{ dB}$$

$$RL_{output} = 10 \log_{10} \frac{1}{|\Gamma_L|^2} = 9.54 \text{ dB.}$$

⑦ $V_o^+ = V_g \frac{Z_{in}}{Z_{in} + Z_g} \frac{1}{(e^{j\beta l} + \Gamma_L e^{-j\beta l})}$ with $\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$ and $Z_{in} = Z_0 \frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)}$

also $Z_{in} = Z_0 \frac{1 + \Gamma_L e^{-j2\beta l}}{1 - \Gamma_L e^{-j2\beta l}} \Rightarrow V_o^+ = V_g \frac{Z_0 \frac{1 + \Gamma_L e^{-j2\beta l}}{1 - \Gamma_L e^{-j2\beta l}}}{(Z_0 \frac{1 + \Gamma_L e^{-j2\beta l}}{1 - \Gamma_L e^{-j2\beta l}} + Z_g) (e^{j\beta l} + \Gamma_L e^{-j\beta l})}$

$$\Rightarrow V_o^+ = V_g \frac{Z_0 \frac{1 + \Gamma_L e^{-j2\beta l}}{1 - \Gamma_L e^{-j2\beta l}}}{\left[\frac{Z_0 + Z_0 \Gamma_L e^{-j2\beta l}}{1 - \Gamma_L e^{-j2\beta l}} + Z_g - Z_g \Gamma_L e^{-j2\beta l} \right] e^{j\beta l} (1 + \Gamma_L e^{-j2\beta l})} = V_g \frac{Z_0 e^{-j\beta l}}{(Z_0 + Z_g) + (Z_0 - Z_g) \Gamma_L e^{-j2\beta l}}$$

$$\Rightarrow V_o^+ = V_g \frac{Z_0 e^{-j\beta l}}{(Z_0 + Z_g) \left[1 + \frac{Z_0 - Z_g}{Z_0 + Z_g} \Gamma_L e^{-j2\beta l} \right]} \Rightarrow V_o^+ = V_g \frac{Z_0}{Z_0 + Z_g} \frac{e^{-j\beta l}}{[1 - \Gamma_L \Gamma_g e^{-j2\beta l}]}$$

where $\Gamma_g = \frac{Z_g - Z_0}{Z_g + Z_0}$