

① $Z_0 = 50 \Omega$ start with an initial guess of $\frac{W}{d} > 2 \Rightarrow B = \frac{377\pi}{2Z_0\sqrt{\epsilon_r}} = 7.985$

then $\frac{W}{d} = \frac{2}{\pi} \left[B - 1 - \ln(2B - 1) + \frac{\epsilon_r - 1}{2\epsilon_r} \left\{ \ln(B - 1) + 0.39 - \frac{0.61}{\epsilon_r} \right\} \right] = 3.081$

so $\frac{W}{d} > 2$ (If $\frac{W}{d}$ turns out to be less than 2, you should use the other expression)

$\Rightarrow \frac{W}{d} = 3.081 \Rightarrow W = 3.081d = 0.391 \text{ cm}$

$\epsilon_e = \frac{\epsilon_r + 1}{2} + \frac{\epsilon_r - 1}{2} \frac{1}{\sqrt{1 + 12d/W}} \Rightarrow \epsilon_e = 1.87$ - Then $\phi = \beta l = k_0 \sqrt{\epsilon_e} l = \frac{2\pi f}{c} l \sqrt{1.87} = 90^\circ$
 $\Rightarrow l = 2.19 \text{ cm}$

② $\beta_z = \beta = \sqrt{k_0^2 - k_c^2} = \sqrt{\left(\frac{\omega}{c}\right)^2 - k_c^2} \Rightarrow \frac{d\beta}{d\omega} = \frac{\omega/c^2}{\sqrt{\left(\frac{\omega}{c}\right)^2 - k_c^2}} = \frac{k_0}{c\beta}$

$\Rightarrow v_g = \left(\frac{d\beta}{d\omega}\right)^{-1} = \frac{c\beta}{k_0}$, $v_p = \frac{\omega}{\beta} = \frac{k_0 c}{\beta}$

③ $\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$ and $\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$

Z-parameters:

$z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} \Rightarrow z_{11} = Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \Big|_{Z_L=\infty} \Rightarrow z_{11} = -jZ_0 \cot \beta l$, $z_{22} = z_{11} = -jZ_0 \cot \beta l$

$z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} \Rightarrow V(z) = V^+ e^{-j\beta z} + V^- e^{j\beta z}$
 $I(z) = \frac{V^+}{Z_0} e^{-j\beta z} - \frac{V^-}{Z_0} e^{j\beta z} \Rightarrow I(0) = I_1 = 0 = \frac{V^+}{Z_0} - \frac{V^-}{Z_0} \Rightarrow V^+ = V^-$

$I(z=l) = \frac{V^+}{Z_0} (e^{-j\beta l} - e^{j\beta l}) = -I_2 \Rightarrow V^+ = \frac{-I_2 Z_0}{(e^{-j\beta l} - e^{j\beta l})} \Rightarrow V^+ = \frac{I_2 Z_0}{2j \sin \beta l}$

$V(z=0) = V_1 = 2V^+ = \frac{2I_2 Z_0}{2j \sin \beta l}$

$\Rightarrow \frac{V_1}{I_2} \Big|_{I_1=0} = \frac{2I_2 Z_0 / 2j \sin \beta l}{I_2} \Rightarrow z_{12} = \frac{Z_0}{j \sin \beta l}$ $z_{21} = z_{12} = \frac{Z_0}{j \sin \beta l}$

Y-parameters:

$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} = -jY_0 \cot \beta l = Y_{22}$

$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$ $V(z=0) = V_1 = 0 \Rightarrow V^+ = -V^-$
 $I(z=0) = I_1 = \frac{2V^+}{Z_0} \Rightarrow V^+ = \frac{Z_0 I_1}{2}$

$V(z=l) = V_2 = V^+ (e^{-j\beta l} - e^{j\beta l})$
 $\Rightarrow V_2 = \frac{Z_0 I_1}{2} (-2j \sin \beta l)$

$$\Rightarrow Y_{12} = Y_{21} = \frac{I_1}{\frac{Z_0 I_1}{2} (-2j \sin \beta l)}$$

$$\Rightarrow \boxed{\frac{j Y_0}{\sin \beta l} = Y_{12} = Y_{21}} \quad (2)$$

where $Y_0 = \frac{1}{Z_0}$

Note that (1) $Z_{in} = Z_0 \frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l}$, $Y_{in} = \frac{1}{Z_{in}} = Y_0 \frac{Z_0 + j Z_L \tan \beta l}{Z_L + j Z_0 \tan \beta l} = Y_0 \frac{\frac{1}{Y_0} + j \frac{1}{Y_L} \tan \beta l}{\frac{1}{Y_L} + j \frac{1}{Y_0} \tan \beta l}$

$$\Rightarrow Y_{in} = Y_0 \frac{Y_L + j Y_0 \tan \beta l}{Y_0 + j Y_L \tan \beta l}$$

(2) When the Z & Y parameters of a transmission line segment is investigated, we notice that to obtain Y parameters, one can use the expressions for the Z -parameters (same equations apply) by replacing Z_{11} by Y_{11} and Z_0 by Y_0 , etc.

(4) $Z_0 = 1$ and using the results of (3)

(a) $Z_{11} = Z_1 - j \cot \beta l$

$Z_{22} = Z_2 - j \cot \beta l$

$Z_{12} = \frac{1}{j \sin \beta l}$

(b) if $\beta l = \frac{\pi}{2} \Rightarrow Z_{11} = Z_1$

$Z_{22} = Z_2$

$Z_{12} = -j$